

AES731 Electrical Technology I

Midterm Exam AY2016-2017 Semester 1

Formulas, Data and Conversions

General

$$e = -1.6 \times 10^{-19} \text{ C}$$

$$1 \text{ hp} = 746 \text{ W}$$

$$1 \text{ rpm} = \frac{2\pi}{60} \text{ rad/s}$$

Electric Fields

$$F = k \frac{q_1 q_2}{d^2}; k = 9.1 \times 10^9 \text{ Nm}^2/\text{C}^2$$

$$E = \frac{F}{q} = \frac{V}{d}$$

$$V = \frac{E}{Q}$$

$$I = \frac{Q}{t}$$

Kirchhoff's Laws

$$\sum I_{\text{node}} = 0$$

$$\sum V_{\text{loop}} = 0$$

Y-Δ conversions

$$R_a = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

Inductors and Capacitors

$$CEMF = -L \frac{\Delta I}{\Delta t}$$

$$T_L = \frac{L}{R}$$

$$V = L \frac{\Delta I}{\Delta t}$$

$$C = \frac{Q}{V}$$

$$C = k \frac{A}{d}; k = 8.85 \times 10^{-12} \text{ F/m}$$

DC Generators

$$E_g = k\phi N$$

DC Motors

$$T = k\phi I_a$$

$$E_{CEMF} = k\phi N$$

Batteries

$$\text{Battery Rating} = \frac{SG_{FC} - SG_{DR}}{\text{Normal Gravity Drop} \times 0.001} \times 100\%$$

Uniformly Accelerated Rotational Motion

$$\omega = \omega_0 + \alpha t$$

$$\omega^2 = \omega_0^2 + 2\alpha\Delta\theta$$

$$\Delta\theta = \omega_0 t + \frac{1}{2}\alpha t^2$$

- 1 Two isolated point charges $q_1 = -50 \text{ nC}$ and $q_2 = +80 \text{ nC}$ are 2.0 mm apart in air as shown in **Figure 1**.



Figure 1

- (a) Sketch the electric field line in the region between and around the charges. [3]
(b) Determine the force acting on the negative charge due to the electric field. [3]

- (c) State and explain whether this electric field is uniform or non-uniform. [2]

.....
.....

- 2** Two parallel conducting plates are held at a distance of 2.0 cm. The plates are connected to a DC power supply making the upper plate 200 V higher than the lower plate.
- (a)** Calculate the electric field strength between the plates. [2]
- (b)** Calculate the force on an electron positioned half way between the plates. [2]
- (c)** Another electron is much closer to the positive plate. Explain why the force on this second is the same as the first one. [1]
-
-
- (d)** The plates are placed in a radiation field that ionizes the air and release a large of electrons between the plates. The plates collect the electrons at a rate of 10^{15} electrons per second. The collected electrons are measured as current in the external circuit. Calculate the magnitude of this current. [2]

- 3 A DC power source is connected to two resistors as shown in **Figure 3**.


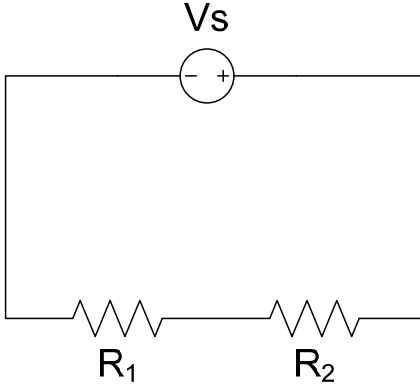


Figure 3

- (a) On **Figure 3**, show the direction of the conventional current. [1]
- (b) Explain whether resistors R_1 and R_2 are connected in series or in parallel. [2]
-
-
- (c) Mark the polarity of each resistor. [2]
- (d) Given that $R_1 = 20 \Omega$ and $R_2 = 40 \Omega$, calculate their equivalent resistance, R_{eq} . [1]
- (e) Given that $V_s = 12 V$, calculate the current in the circuit. [1]
- (f) Calculate the potential drop across each resistor. [2]


- 4 Find the equivalent resistance for each of the following resistive networks. Each resistor has a value of $60\ \Omega$.

(a)

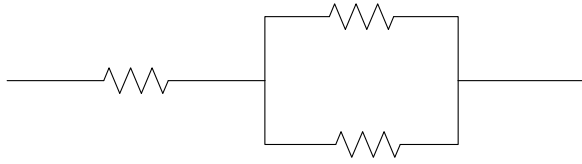

[2]

(b)

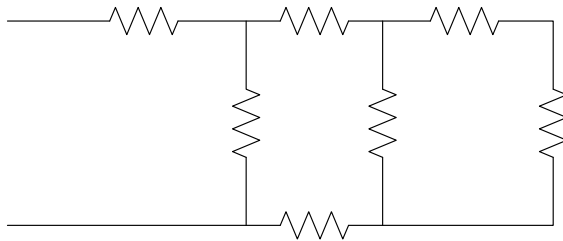

[4]

- 5 Given the circuit shown in **Figure 5**, follow steps (a) through (f) to solve the circuit using mesh analysis, where $V_A = 20\text{ V}$, $V_B = 10\text{ V}$, $R_1 = 5\ \Omega$, $R_2 = 15\ \Omega$ AND $R_3 = 10\ \Omega$.

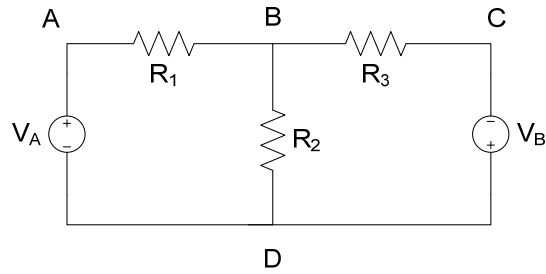


Figure 5

- (a) Assuming the currents in loops ABDA (loops 1) and BCDB (loop 2) are clockwise, assign a voltage for each resistor and mark its polarity. [2]
- (b) Write a KVL equation for each loop 1. [2]
- (c) Use Ohm's law to rewrite the equation in (b) in terms of current and resistance. [2]
- (d) Repeat steps (b) and (c) for loop 2. [2]
- (e) Solve the current equations you obtained in (c) and (d) for loop currents. (You may do so using a calculator and not show working for this step.) [2]
- (f) Calculate all unknown voltages in the circuit. [3]

- 6 Given the circuit shown in **Figure 6**, follow steps **(a)** through **(f)** to solve the circuit using node analysis, where $V_A = 20\text{ V}$, $V_B = 30\text{ V}$, $R_1 = 10\ \Omega$, $R_2 = 30\ \Omega$ AND $R_3 = 15\ \Omega$.

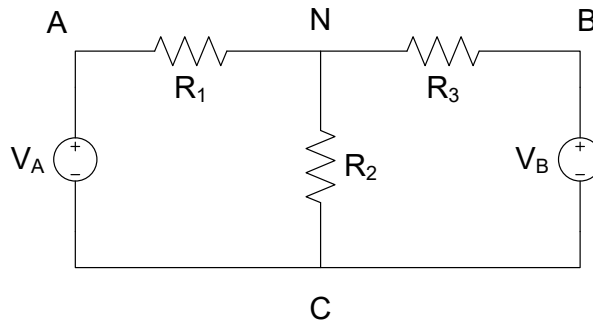


Figure 6

- (a)** Write a KCL equation for node N. [2]
- (b)** Rewrite your equation from **(a)** using element voltages. [2]
- (c)** Taking node C as reference node, rewrite your equation from **(b)** using node voltages. [2]
- (d)** Solve for all unknown node *and* element voltages. [3]
- (e)** Determine all branch currents. [3]